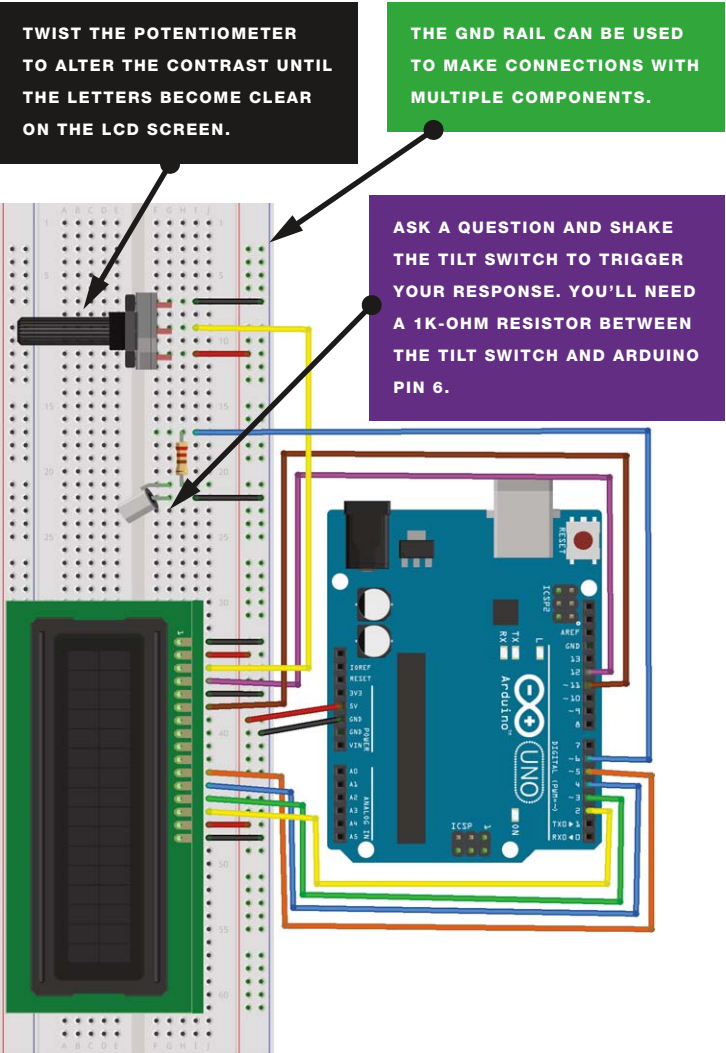


| TILT BALL SWITCH | ARDUINO                      |
|------------------|------------------------------|
| Leg 1            | Pin 6 via<br>1k-ohm resistor |
| Leg 2            | GND                          |

6. Connect your breadboard rails to the Arduino +5V and GND for power.
7. Confirm that your setup matches Figure 14-3, and upload the code in “The Sketch” on page 122.



**FIGURE 14-3:**  
The circuit diagram  
for the fortune teller