## FIGURE 1-4:

Circuit diagram for the pushbutton-controlled LED

THE PUSHBUTTON IS CONNECTED TO PIN 2. PRESS THIS BUTTON TO TURN ON THE LED. THE LED WILL STAY LIT ONLY FOR THE DURATION THAT THE BUTTON IS PRESSED.

